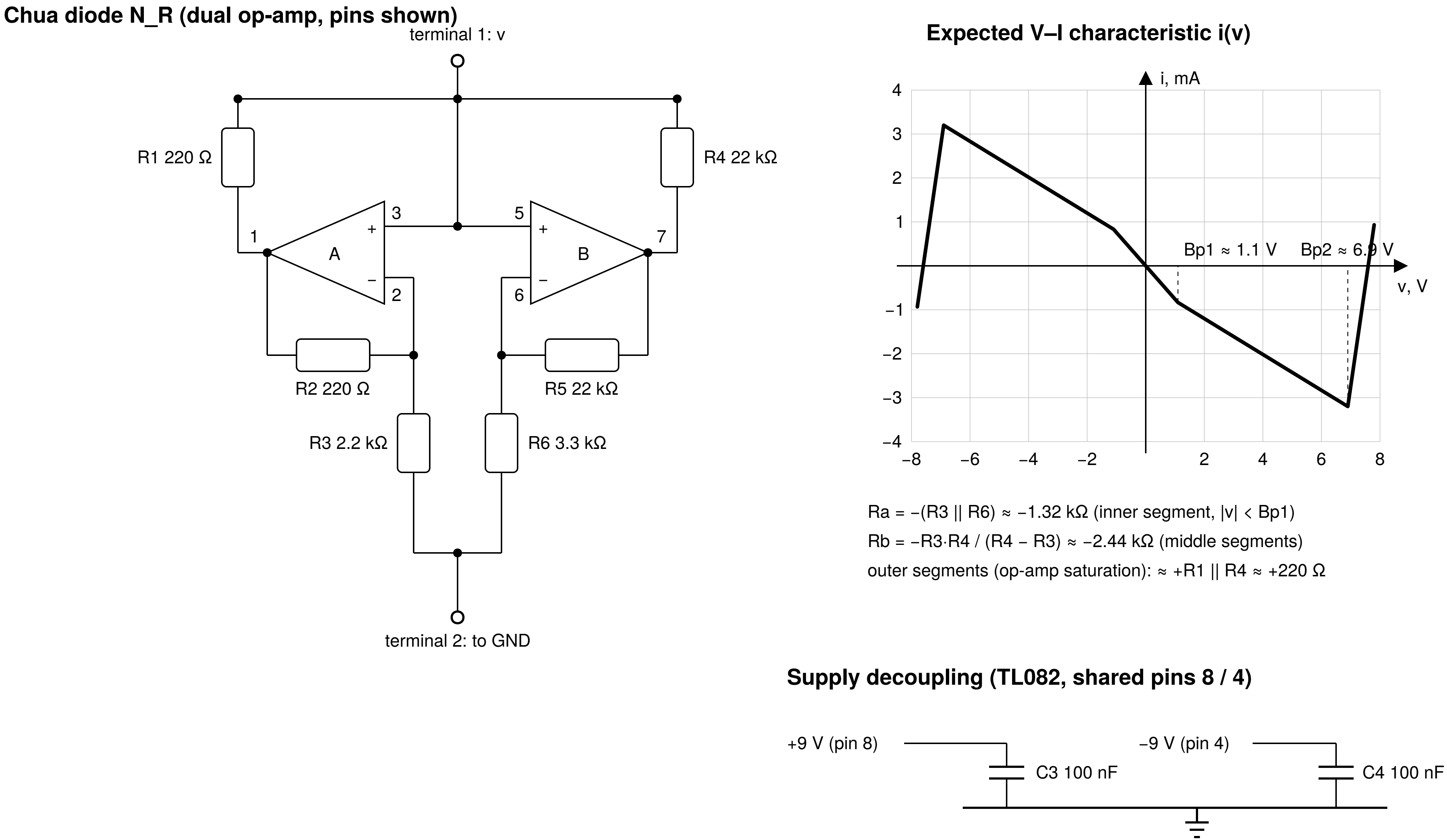

Fig. 1. Chua diode as a two-terminal element: circuit, expected piecewise-linear V–I curve, and supply decoupling.

Chua oscillator (N_R shown as a two-terminal element)

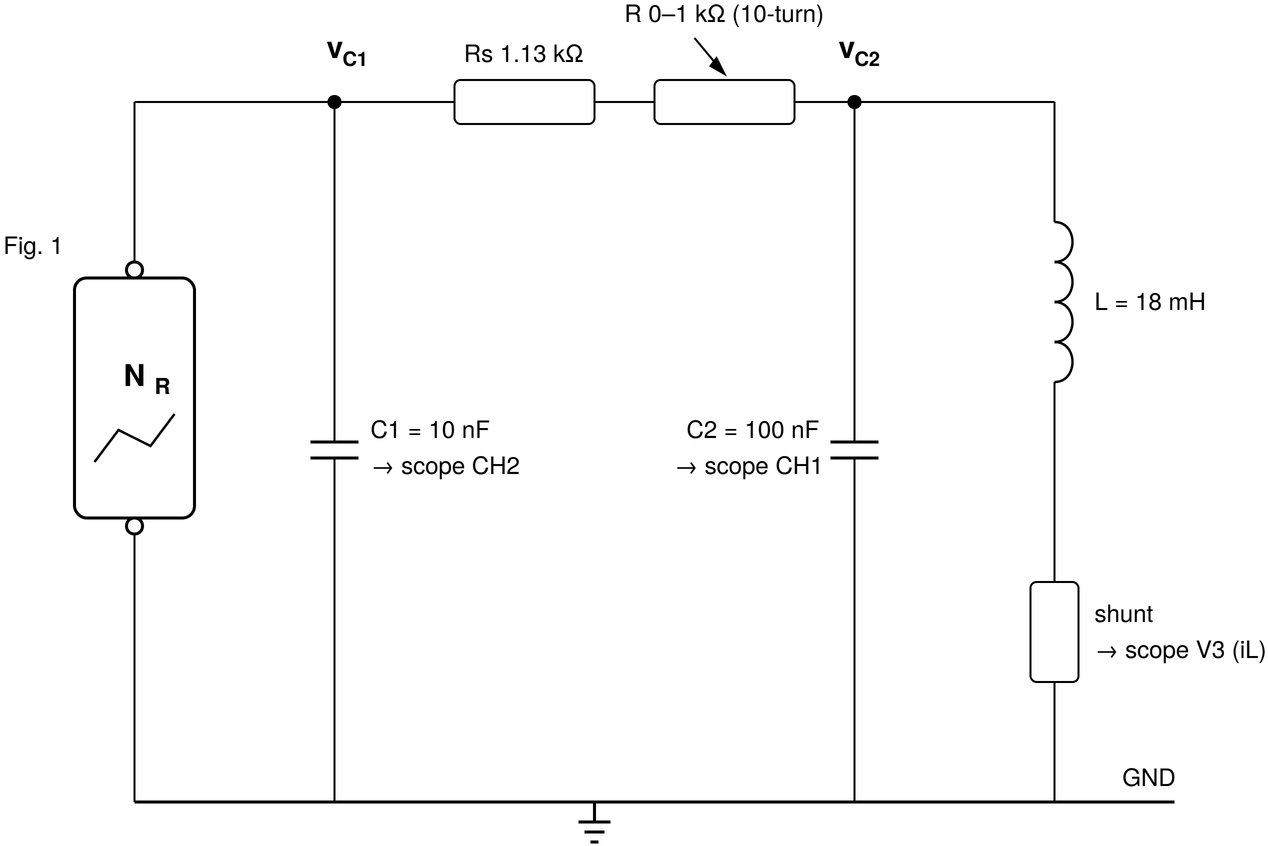

Total coupling resistance R_total = Rs + R = 1.13…2.13 kΩ; measurement points: 1.54 / 1.74 / 1.91 kΩ.

Dimensionless parameters: $\alpha = C2/C1 = 10$, $\beta = R\_total^2 \cdot C2/L = 13 \ldots 20$.

Fig. 2. Chua oscillator: linear resonant part (L, C2), coupling resistance, C1, and the nonlinear element N_R of Fig. 1.